

A Fully Compositional Theory of Digital Circuits


George Kaye

University of Birmingham

15 February 2024 – PPLV Research Seminar


What are we going to be talking about?

Digital circuits!

 


What are we going to be talking about?

Digital circuits!

 

What are we going to be talking about?

 We want a **compositional** theory of digital circuits.



Using **string diagrams** removes
much of the bureaucracy

(also they look pretty)

How did we get here?



2003



Yves Lafont

'Towards an algebraic theory of Boolean circuits'

2016

The story so far



Dan Ghica, Achim Jung, Aliaume Lopez

'Diagrammatic semantics for digital circuits'

The story so far



'Wow, this guy seems pretty groovy'



OCaml noises

2019

The story so far



'No'
'Okay'



'Do you know category theory'
'Do you want to do circuits stuff'

2021

The story so far



+




=




+



=

 


 

David Sprunger


(now at Indiana State University)

Let's get dangerous

 


Combinational circuit components


gates

 

AND gate

 

OR gate

 

NOT gate

(co)monoid structure



disconnected



fork



join



stub

categorical structure



identity



symmetry

Light circuits



only contain gates and structure.

(actually, we do it more generally than this, but let's keep it simple)

Sequential circuit components

Values



false



true




short circuit

Delay



Feedback

 


Dark circuits





may contain delay or feedback.

 Circuits are morphisms in a **freely generated symmetric traced monoidal category** (STMC).



Need an example?



 
 


What is the meaning?

Denotational semantics

Interpreting the values

Values are interpreted in a **lattice**:

    

Let's make everything a function



monotone functions

$$\bar{g}: \mathbf{V}^m \rightarrow \mathbf{V}$$



initialise

$$() \mapsto (\perp)$$



copy

$$x \mapsto (x, x)$$



join in the lattice

$$(x, y) \mapsto x \sqcup y$$



discard

$$x \mapsto ()$$

Feedback is interpreted as the **least fixed point**.

How do we model **delay**?

Streams!

A **stream** $\mathbf{V}^\omega$ is an infinite sequence of values.

$$V_0 :: V_1 :: V_2 :: V_3 :: V_4 :: V_5 :: V_6 :: V_7 :: \dots$$

A **stream function** $\mathbf{V}^\omega \rightarrow \mathbf{V}^\omega$ consumes and produces streams.

$$f(V_0 :: V_1 :: V_2 :: V_3 :: V_4 :: \dots) = W_0 :: W_1 :: W_2 :: W_3 :: W_4 :: \dots$$

Interpreting the sequential components

$$\boxed{v} \vdash () := v :: \perp :: \perp :: \perp :: \dots$$

$$\vdash \boxed{\triangleright} (v_0 :: v_1 :: v_2 :: \dots) := \perp :: v_0 :: v_1 :: v_2 :: \dots$$

Does every stream function $(\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$
correspond to a circuit?

No.

(but this is to be expected!)

Restricting the stream functions

Circuits are **causal**.

They can only depend **what they've seen so far**.

Circuits are **monotone**.

They are constructed from **monotone functions**.

Is that all? **Not quite...** (but we'll get there)

Some operations on stream functions

Given a causal stream function $f: (\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$ and an element $a \in \mathbf{V}^m$...


initial output $f[a] \in \mathbf{V}^n$

‘the first thing f produces given a ’

stream derivative $f_a \in (\mathbf{V}^m)^\omega \rightarrow (\mathbf{V}^n)^\omega$

‘how f behaves after seeing a first’

Hold on, these look familiar...

 

Mealy machines!

Stream functions are the *states* in a Mealy machine.

Circuits have finitely many behaviours

Circuits have a finite number of components.

So there are finite number of states in the Mealy machine.

So the outputs of streams given some input must be **periodic**.

(There are finitely many **stream derivatives**).

These are the streams we're looking for

Theorem

A stream function is the interpretation of a sequential circuit if and only if it is causal, monotone and has finitely many stream derivatives.

Sound and complete denotational semantics

Suppose we have two circuits
with the same denotation


$$\llbracket - \boxed{F} - \rrbracket = \llbracket - \boxed{G} - \rrbracket$$

What does this tell us about the
structure of these circuits?

Operational semantics


We want to find a set of
reductions for digital circuits

 We want to reduce circuits to their outputs
syntactically in a **step-by-step** manner



by moving boxes and wires around

Going global

 


The sticking point

What are we going to do about the non-delay-guarded trace?

In industry, feedback is usually **delay-guarded**.

 But this rules out some **clever** circuits!




(And also it would be cheating)

$\mathbf{V}$ is a **finite** lattice...


The functions are monotone...

We can compute the **least fixed point**
in finite iterations!

 Getting rid of non-delay-guarded feedback



 Getting rid of non-delay-guarded feedback



For **any** circuit




What is the goal

We want to compute the **outputs** of circuits given some **inputs**



How does a circuit **process** a value?

Reducing values

 


47


Lemma

For every $\boxed{F}$ there exists $\boxed{\bar{w}}$ s.t. $\boxed{\bar{v}} \boxed{F} \rightsquigarrow \boxed{\bar{w}}$.

What about **delays**?

 

Catching the jet stream

 

When are two circuits **observationally equivalent**?

Circuits have **finitely many states**...

Definition

Two circuits with at most c delay components are observationally equivalent if the reduction procedure creates the same outputs for all inputs of length $|\mathbf{V}|^c + 1$.

Theorem

Two circuits are observationally equivalent if and only if they are denotationally equivalent.


Sound and complete **operational semantics**

This is a **superexponential** upper bound for testing
circuit equivalence

Can we do better?

Algebraic semantics

First things first...

 


We want a way to use equations to translate a circuit into another circuit with the same behaviour

Say we have a procedure $|\text{---}|$ for establishing a
canonical circuit for a function $f: \mathbf{V}^m \rightarrow \mathbf{V}^n$

A circuit is **normalised** if it is in the image of $|\text{---}|$


What equations are needed to
normalise any circuit?

It's completely normal

 

It's completely normal


Is this enough?

 


The cores may **not** have the same semantics!

Idea: **encode** circuits so their state words have length equal to the number of states

 
Need to know the number of states: **isolate** the state transition and output



 
Need equations to make the fork **natural** and **unital**



Cartesian doubt

 

Now add an **encoding** equation

 

(I'm hiding some of the internal machinations here)

By the completeness of the denotational semantics, each stream function has a corresponding **encoded** circuit...


Theorem

Two circuits are equal by the equations if and only if they are denotationally equal.

Sound and complete **algebraic semantics**


Graph rewriting

Making it combinatorial

 


It is **hard** for computers to work with string diagrams...
...but computers **love** graphs!


A hyper kind of graph

 

 There are correspondences between **certain classes of hypergraphs** and **circuit string diagrams**.



Using the correspondence

 


The rewriting framework has been *implemented* in a
hardware description language.



(the language is still in development)
(so I've been warned not to accidentally announce anything)
(also they changed everything so I can't actually compile it at the moment)


I can still show you something

Create a circuit...

 



I can still show you something

 The evaluator converts it into Mealy form...




I can still show you something

...and then evaluates an input.

  

 Three different semantics for sequential digital circuits



Can adapt for automatic reasoning using **graph rewriting**